

Experiment 2 – Fixed , Dynamic Arrays and Queues

Part 1:

Aim:

Write the code to design a D Flip Flop and write test bench in System Verilog.

Code:

DUT:

```
module dff(input d,clk, output reg q);
    always@(posedge clk) q<=d;
endmodule
```

TB:

```
module tb();
    bit d,clk,q,y;
    dff duv(d,clk,q);
    int x = 0;

    initial forever #5 clk = !clk;

    initial begin
        repeat(10)begin
            @(negedge clk) begin
                d <= $random;y <= d;
            end

            @(posedge clk) if(q != y) x = x+1;
            $display("%0d ip is %d op is %d",$time,d,q);
        end
        if(!x) $display("Success"); else $display("Failure");
    end
endmodule
```

Output

```
# KERNEL: 15 ip is 0 op is 0
# KERNEL: 25 ip is 1 op is 0
# KERNEL: 35 ip is 1 op is 1
# KERNEL: 45 ip is 1 op is 1
# KERNEL: 55 ip is 1 op is 1
# KERNEL: 65 ip is 1 op is 1
# KERNEL: 75 ip is 1 op is 1
# KERNEL: 85 ip is 0 op is 1
# KERNEL: 95 ip is 1 op is 0
# KERNEL: 105 ip is 1 op is 1
# KERNEL: Success
```

Part 2:

Aim:

Write the code to design a 4 bit adder and write its test bench in System Verilog

Code:

DUT:

```
module add(input [3:0] a,b, input cin, output [3:0] sum, output cout);  
    assign {cout,sum} = a+b+cin;  
endmodule
```

TB:

```
module tb();  
    reg [3:0] a,b;  
    wire [3:0] sum;  
    reg cin;  
    wire cout;  
    int x=0;  
  
    add duv(a,b,cin,sum,cout);  
  
    initial begin  
        repeat(10) begin  
            {a,b,cin} = $random;  
            #1;  
            if({cout,sum} != a+b+cin) x = x+1;  
            $display("ip is %d,%d, %b op is %d",a,b,cin,{cout,sum});  
        end  
        if(!x) $display("Success");  
        else $display("Failure");  
    end  
endmodule
```

Output:

```
# KERNEL: ip is  9, 2, 0 op is 11  
# KERNEL: ip is  4, 0, 1 op is  5  
# KERNEL: ip is  0, 4, 1 op is  5  
# KERNEL: ip is  3, 1, 1 op is  5  
# KERNEL: ip is  8, 6, 1 op is 15  
# KERNEL: ip is 12, 6, 1 op is 19  
# KERNEL: ip is  3, 2, 1 op is  6  
# KERNEL: ip is  0, 9, 0 op is  9  
# KERNEL: ip is  8, 0, 1 op is  9  
# KERNEL: ip is  8, 6, 1 op is 15  
# KERNEL: Success
```

Result:

The given problem statement is executed and verified to be correct.